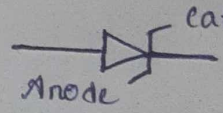


ALL ABOUT ZENER DIODES

★ ZENER DIODES


- Zener diodes are silicon based semiconductor devices which allow current to flow bidirectionally either reverse or forward.
- It is comprised of heavily doped P-N silicon junction.
- It has a ~~reset~~ reverse breakdown voltage which when achieved; diode starts to conduct current in reverse direction.
- One of the main advantage of Zener diode is that a varying range of voltages will still maintain a constant voltage drop across the diode. As a result, Zener diodes can be used for voltage regulation purposes.
- It is denoted by the symbol \rightarrow 

★ ZENER DIODE SPECIFICATIONS

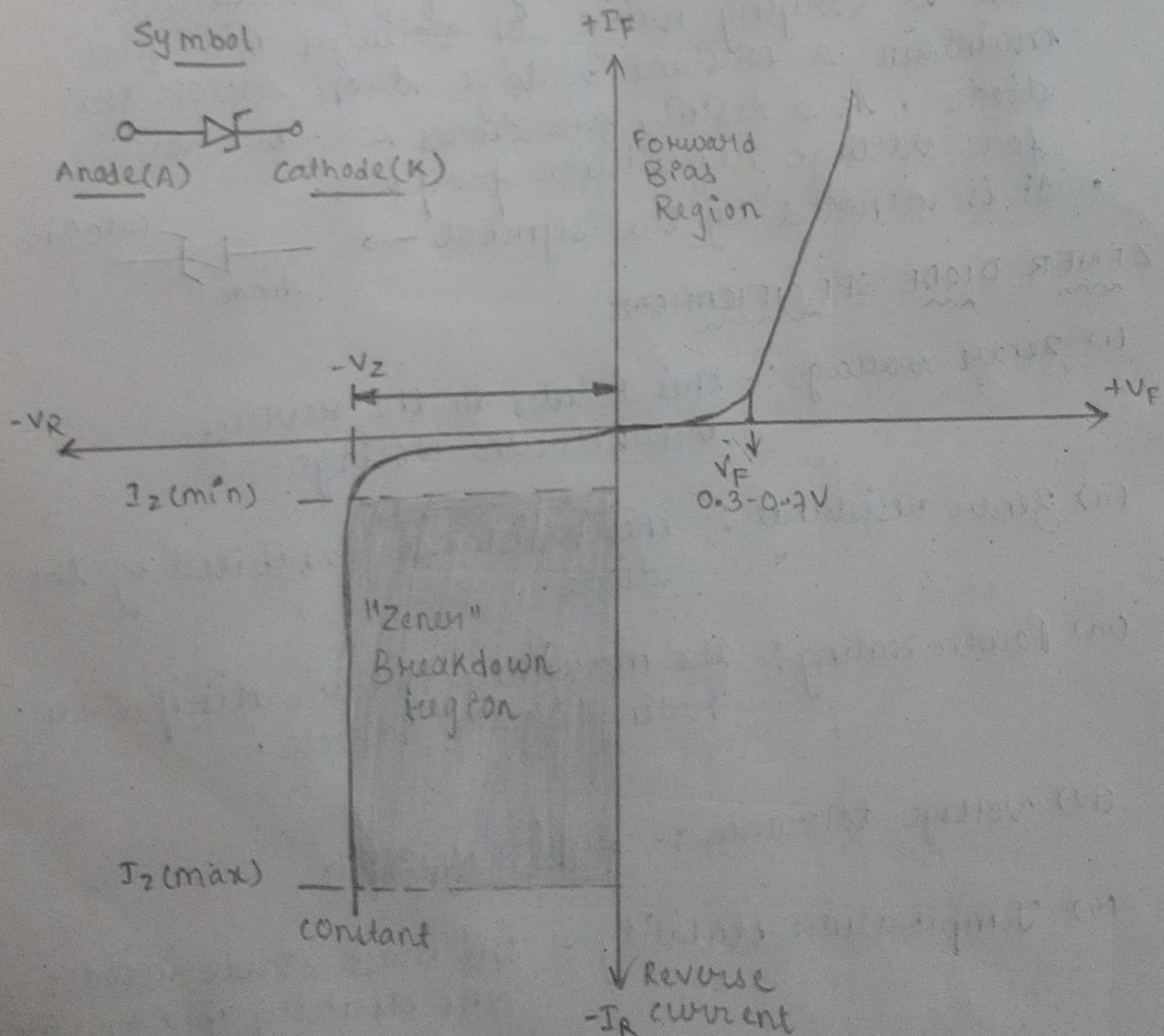- (i) Zener voltage:- this relates to the reverse breakdown voltage.
- (ii) Zener resistance:- the resistance exhibited by the diode.
- (iii) Power rating:- the maximum power dissipation rating of the diode.
- (iv) Voltage tolerance:- typically $\pm 5\%$.
- (v) Temperature stability:- the most stable diodes are usually approx. 5V.

★ ZENER DIODE CHARACTERISTICS

- Zener diodes operate similarly to conventional diodes when in the forward-bias mode. They have a bias turn on voltage of between $0.3-0.7V$.
- In the reverse bias mode, when the voltage reaches the set breakdown voltage the reverse current characteristic change abruptly to a comparatively high level and no matter how much is the applied voltage, the voltage drop across zener diode remains constant in the breakdown region.
- Characteristic sketch




★ ZENER DIODE APPLICATIONS

- (i) Voltage Regulation (#)
- (ii) Voltage Reference
- (iii) Surge suppression
- (iv) switching applications
- (v) clipper circuits.

• ZENER DIODE AS A VOLTAGE REGULATOR.

Basic configuration:

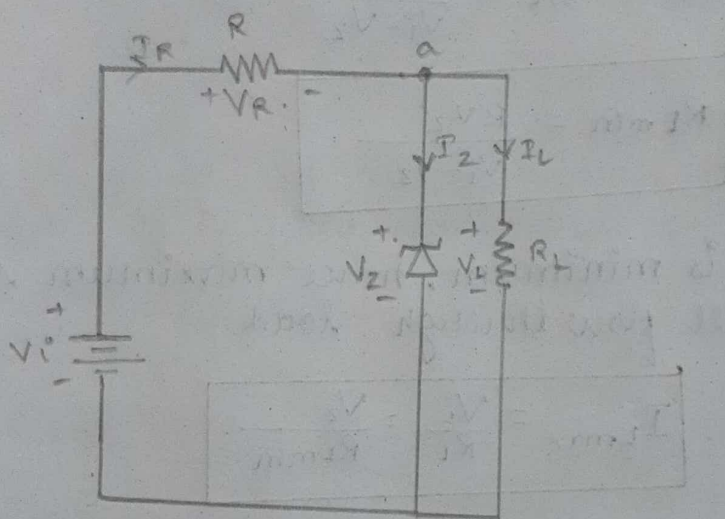

Case 1: Both V_i and R_L Fixed.

∵ Diode is parallel to load.

$$\therefore V_Z = V_L$$

On applying voltage divider rule, we have

$$V_Z = V_L = \frac{R_L V_i}{R_L + R}$$

on applying KCL at node a, we have.

$$I_R = I_Z + I_L$$

$$\Rightarrow I_Z = I_R - I_L$$

$$I_L = \frac{V_L}{R_L} \quad \text{and} \quad I_R = \frac{V_R}{R} = \frac{V_i - V_L}{R}$$

$$P_Z = V_Z I_Z$$

Case 2: V_i is fixed and R_L is variable.

We know, from voltage divider rule,

$$V_L = V_Z = \frac{R_L V_i}{R_L + R}$$

$$\Rightarrow \frac{R_L + R}{R_L} = \frac{V_i}{V_Z}$$

$$\Rightarrow 1 + \frac{R}{R_L} = \frac{V_i}{V_Z}$$

$$\Rightarrow \frac{R}{R_L} = \frac{V_i}{V_Z} - 1 = \frac{V_i - V_Z}{V_Z}$$

$$\Rightarrow R_L = \frac{R V_Z}{V_i - V_Z}$$

OH,

$$R_{L \min} = \frac{R V_Z}{V_i - V_Z}$$

$\therefore R_L$ is minimum, hence maximum current will flow through load.

$$\therefore I_{L \max} = \frac{V_L}{R_L} = \frac{V_Z}{R_{L \min}}$$

Once the diode is ON, voltage across R is fixed at,

$$V_R = V_i - V_Z$$

$$\therefore I_R = \frac{V_R}{R} = \frac{V_i - V_Z}{R}$$

And, Zener current.

$$I_Z = I_R - I_L$$

$$\therefore I_{L \min} = I_R - I_Z$$

$\therefore I_L$ is minimum, hence R_L is maximum.

$$\therefore R_{L \max} = \frac{V_L}{I_{L \min}} = \frac{V_Z}{I_R - I_Z}$$

Case 3: R_L is fixed and V_i is variable

We know, from voltage divider rule,

$$V_L = V_Z = \frac{R_L V_i}{R_L + R}$$

$$\Rightarrow V_i = \frac{(R_L + R) V_Z}{R_L}$$

$$\text{or, } V_{i\min} = \frac{(R_L + R) V_Z}{R_L}$$

The maximum value of V_i is limited by the maximum zener current $I_{Z\max} = I_R - I_L$

$$I_{R\max} = I_{Z\max} + I_L$$

$\therefore I_L$ is fixed at V_Z / R_L and $I_{Z\max}$ is the maximum value of I_Z , the maximum V_i is defined by.

$$V_{i\max} = V_{R\max} + V_Z$$

$$V_{i\max} = I_{R\max} R + V_Z$$

Question: Determine $R_{L\min}$ and $R_{L\max}$ for the given configuration.

Ans given: $V_i = 50V$, $V_Z = 10V$,
 $I_{Z\max} = 32mA$, $R = 1k\Omega$

$$\begin{aligned} R_{L\min} &= \frac{R V_Z}{V_i - V_Z} = \frac{1000 \times 10}{50 - 10} \\ &= \frac{1000 \times 10}{40} \\ &= \frac{1000}{4} = 250\Omega \end{aligned}$$

$$I_R = \frac{V_R}{R} = \frac{V_i - V_Z}{R} = \frac{40}{1k\Omega} = 40mA$$

$$\therefore I_{L\min} = I_R - I_{Z\max} = 40 - 32 = 8mA$$

$$\therefore R_{L\max} = \frac{V_Z}{I_{L\min}} = \frac{10V}{8mA} = 1.25k\Omega \text{ or } 1250\Omega$$

$$\therefore R_{L\min} = 250\Omega, R_{L\max} = 1.25k\Omega, \text{ or, } 250 \leq R_L \leq 1250$$

