


UNIT - IV

Op-Amp = Operational Amplifier :-

→ Op-Amp is a high gain differential amplifier with very high i/p impedance & very low o/p impedance and used for mathematical operations like addition, subtraction, multiplication, differentiation, integration, exponential operⁿ, log operⁿ etc.

11/11/19

Schematic diagram of OP-amp :-

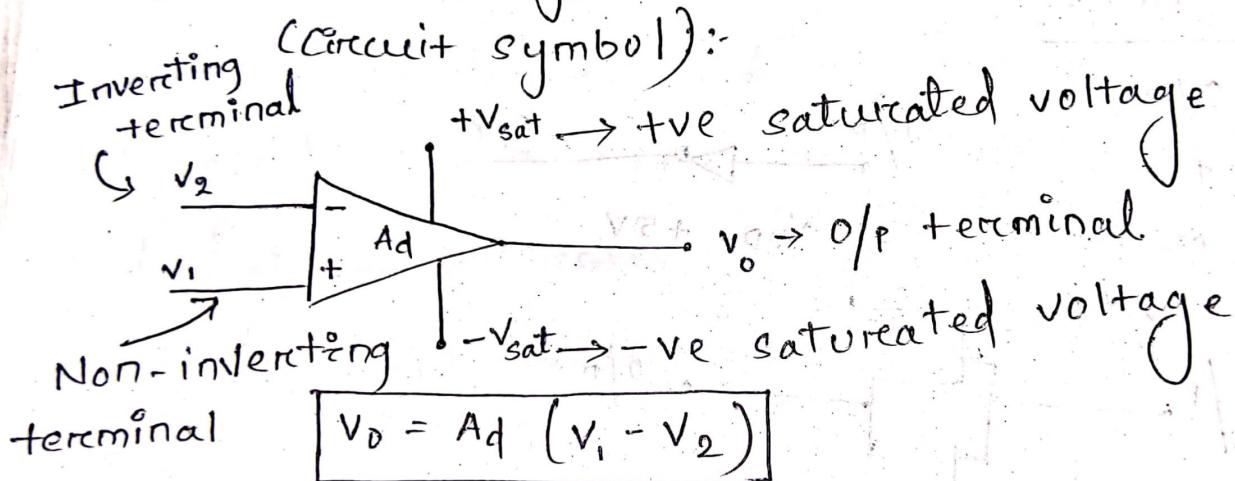

PIN / I_c configuration of OP-amp :-

$$I_c = 741 \text{ off set null}$$

Op-amp - 8 pin I_c pin

Non inverting

I_c

-V_{sat}

1	U	8
2		
3	741	7
4		6
5		5


No-connection

+V_{sat}

O/P

off set null

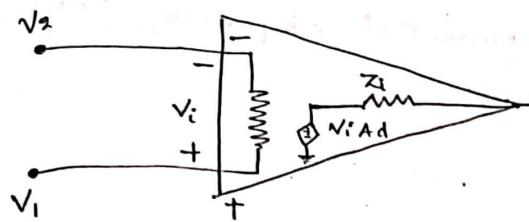
Internal str^c of OP-Amp :- (non-inverting input) with load



Characteristics of ideal OP-AMP :-

- I/P impedance is very high; $Z_i = \infty$
- O/P impedance is very small; $Z_o = 0$
- Voltage gain = very high; $A_d = \infty$
- There is no offset voltage.
- Very high CMRR; $CMRR = \infty$ (common mode rejection ratio)
- Very slow slew rate, slew rate = 0

Transfer characteristics :-

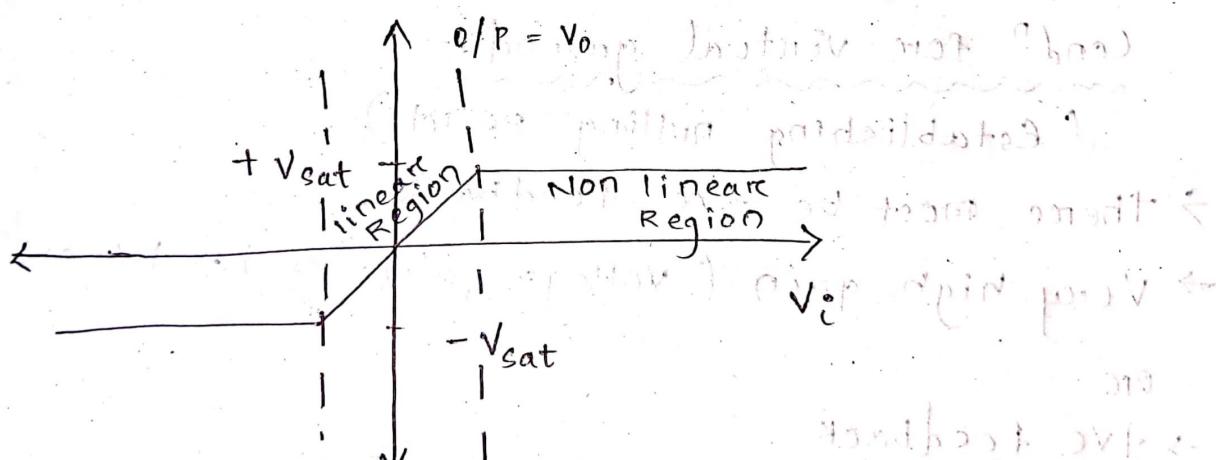

App. of op-Amp in linear region :-

- Inverting amplifier
- Non-inverting amplifier
- Summing amplifier (Adder)
- Subtractor

- Buffer (Voltage "follower")
- Log amplifier
- Antilog amplifier (Exponential amplifier) } optional
- Differential amplifier
- Differentiate
- Integrate
-

Virtual Ground :-

13/11/2019

- Earth surface is equipotential surface, so, the potential diff. betⁿ 2 points on the earth's surface is always 0.
- Ground is also equipotential surface in which each point is having 0V potential. So P.V betⁿ two points on ground is 0V.
- Current into the ground is max^m. (I_{max})
- In case of virtual ground, P.V is 0 and current into the virtual ground is 0A.

Condⁿ for virtual ground :-


(Establishing nulling point)

- There must be -ve feedback.
- Very high gain (Voltage gain = ∞) $\Rightarrow AV = \infty$.

OR

- +ve feedback

- Unit gain ($AV = 1$)

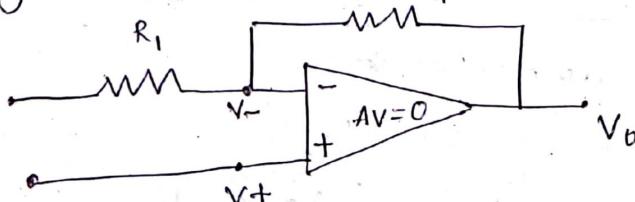


In case of OP-Amp, with -ve feedback and unit gain, that exist virtual ground, betⁿ

inverting & non-inverting terminal.

- In the above fig, $V_+ = V_-$ whence,
 V_+ → Potential at non-inverting terminal.
 V_- → Potential at inverting terminal.

Non-inverting amplifier :-

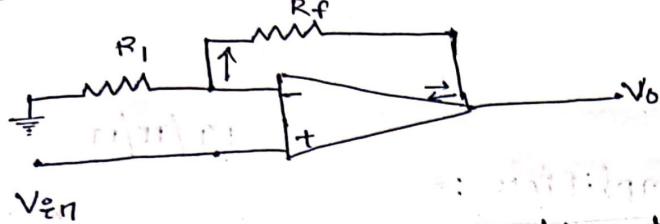


Applying nodal eqn at Inverting terminal :-

$$\frac{V_{in} - 0}{R_1} + \frac{V_{in} - V_0}{R_f} + 0 = 0$$

$$V_0 = \left(1 + \frac{R_f}{R_1}\right) V_{in}$$
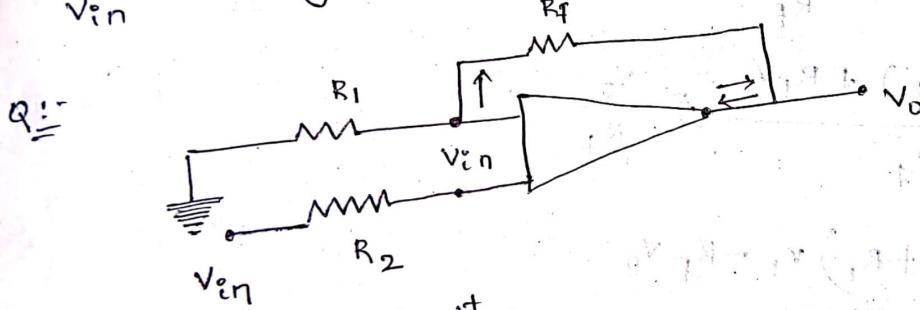
$$\frac{V_0}{V_{in}} = \text{Voltage gain} = \left(1 + \frac{R_f}{R_1}\right)$$




calculate the output.

$$\frac{V_{in} - 0}{R_1} + \frac{V_{in} - V_0}{R_f} + \frac{V_{in} - V_0}{R_f} + 0 = 0$$

$$V_0 = \left(1 + \frac{R_f}{R_1}\right) V_{in}$$

Inverting amplifier:-

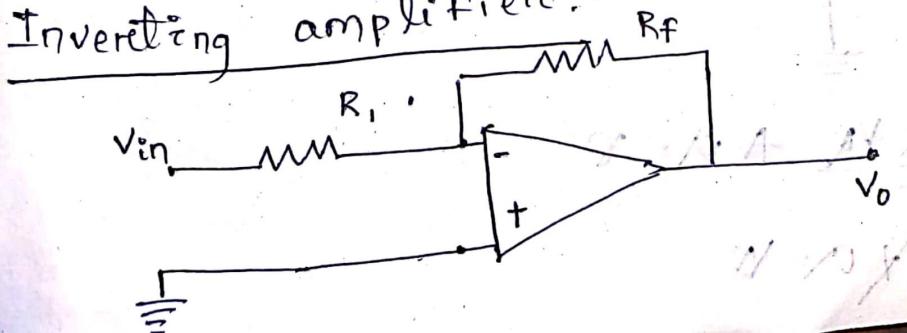

$$\frac{0 - V_{in}}{R_1} + \frac{V_{in} - V_o}{R_f} + 0 = 0$$


$$\Rightarrow \left(\frac{1}{R_1} + \frac{1}{R_f} \right) V_o = V_{in}$$

$$\frac{0 - V_{in}}{R_1} + \frac{0 - V_i}{R_f} = 0$$

$$V_o = -\frac{R_f}{R_1}$$

14/11/19

Differential Amplifier :-

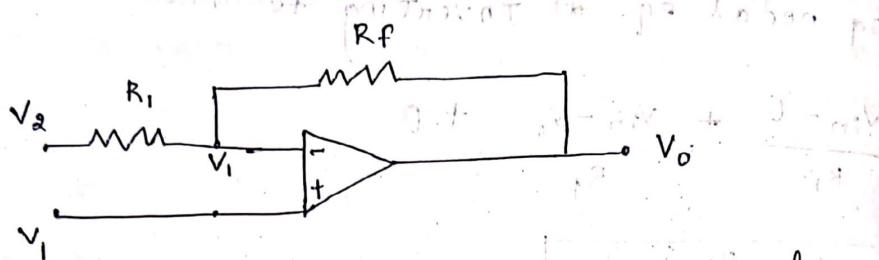


Applying nodal at inverting terminal

$$\frac{V_1 - V_2}{R_1} + \frac{V_1 - V_o}{R_f} + 0 = 0$$

$$\Rightarrow \frac{R_f(V_1 - V_2) + R_1 V_1}{R_1 R_f} = \frac{V_o}{R_f}$$

$$\Rightarrow V_o = \frac{(R_f + R_1)V_1 - R_f V_2}{R_1}$$

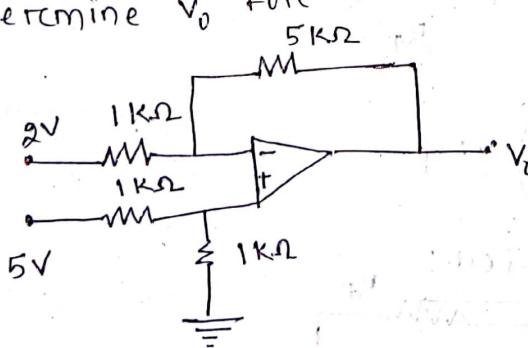Q:- Determine V_o for the following circuit.



$$\frac{5 - 2}{1} + \frac{5 - V_o}{5} + 0 = 0$$

$$\Rightarrow \frac{3}{1} + \left(-\frac{V_o}{5} \right) + 0 = 0$$

$$2.5 = \frac{V_0}{5}$$

$$\Rightarrow V_0 = 12.5$$

$$V_+ = \frac{5 \times 1\text{ k}\Omega}{1\text{ k} + 1\text{ k}\Omega} = \frac{5}{2} \text{ V} = 2.5 \text{ V}$$


$$V_- = \frac{5}{2} \text{ V} = 2.5 \text{ V}$$

Applying nodal at inverting terminal,

$$\frac{2.5 - 2}{1\text{ k}\Omega} + \frac{2.5 - V_0}{5\text{ k}\Omega} + 0 = 0$$

$$\Rightarrow V_0 = 5 \text{ V}$$

Summing Amplifier :- (Adder)

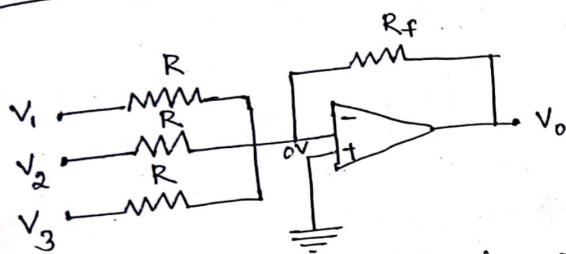


Apply nodal at inverting terminal,

$$\frac{V_1 - V_2}{R} + \frac{V_1 - V_0}{R_f} + \frac{V_2 - V_0}{R} + \frac{V_3 - V_0}{R} + 0 = 0$$

$$\Rightarrow \frac{V_0 - V_0}{R_f} + \left(\frac{-1}{R} \right) (V_1 + V_2 + V_3) = 0$$

$$\Rightarrow V_0 = -R_f (V_1 + V_2 + V_3)$$


Buffer / voltage follower

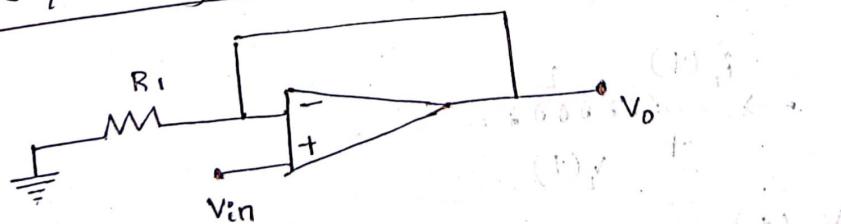

$$V_0 = V_{in}$$

$$\text{gain} = AV = 1$$


Subtractor Amplifier :-

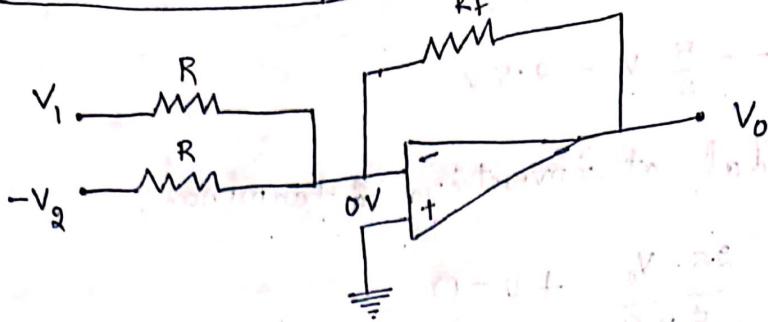

$$\frac{0 - V_0}{R_f} + \frac{0 - V_1}{R} + \frac{0 + V_2}{R} = 0$$

$$V_0 = -\frac{R_f}{R_1} (V_1 - V_2)$$

Note-1

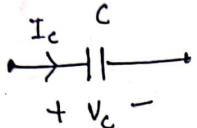

$$I_c = C \frac{dV}{dt}$$

$$\Rightarrow C \frac{dV_c}{dt} = i_c$$


$$\Rightarrow \frac{dV_c}{dt} = \frac{1}{C} i_c$$

$$\Rightarrow \int dV_c = \frac{1}{C} \int i_c dt$$

$$\Rightarrow V_c(t) = \frac{1}{C} \int_{-\infty}^t i_c(t) dt$$

Note-2


Inductor (L)

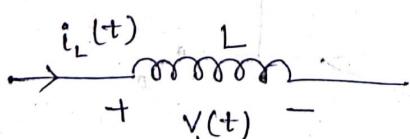

$$V_L(t) = L \frac{di(t)}{dt}$$

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t V_L(t) dt$$

Integrator :-

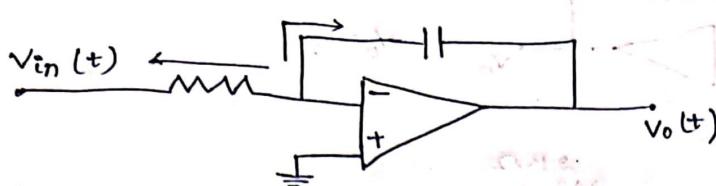


Applying nodal at inverting terminal,

$$\frac{0 - v_{in}(t)}{R} + C \frac{d}{dt}(0 - v_o(t)) + 0 = 0$$

$$\Rightarrow -C \frac{d v_o(t)}{dt} = \frac{v_{in}(t)}{R}$$

$$\Rightarrow \frac{d v_o(t)}{dt} = -\frac{1}{RC} v_{in}(t)$$

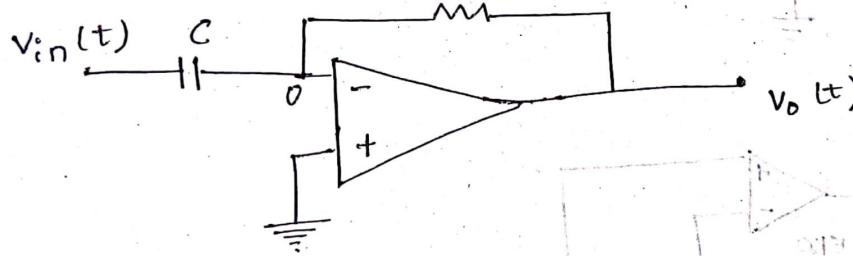
$$\Rightarrow v_o(t) = -\frac{1}{RC} \int_{-\infty}^t v_{in}(t') dt'$$




$$C \frac{d}{dt}(0 - v_{in}(t)) + \frac{0 - v_o(t)}{R} + 0 = 0$$

$$\Rightarrow v_o(t) = -RC \frac{d}{dt} v_{in}(t)$$


Q:- 1)

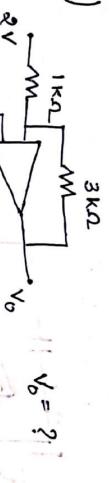


18/11/19

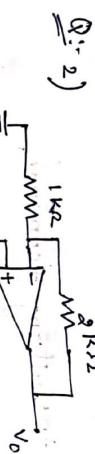

Q:- 3)

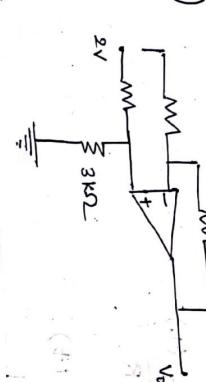


Q:- 4)

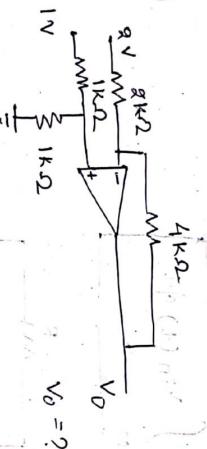

Q:- 5)



Q:- 6)

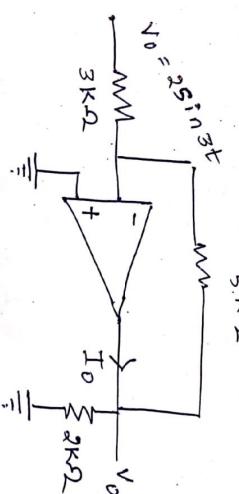

$V_o = ?$

$I_o = ?$

i) Applying nodal at inverting terminal,

$$\frac{D - V_0}{R_F} + \frac{D - V_1}{R} + 0 = D$$

$$\Rightarrow V_0 = -\frac{R_F}{R_1} (V_1 - V_2)$$

$$\Rightarrow V_0 = -\frac{3}{1} (2 - 0)$$

$$\Rightarrow \boxed{V_0 = -6V}$$

ii) Applying nodal at inverting terminal,

$$\frac{V_0}{2+1} = \frac{4 \times 2}{2+1} = \frac{8}{3} = \frac{V_1 - V_2}{2+1}$$

$$V_0 = \frac{1}{2} V = 0.5V$$

$$2) \frac{D - 0}{1K} + \frac{2 - V_0}{2K} + 0 = D$$

$$\Rightarrow -9 \cdot 5 - V_0 = 0 \Rightarrow \boxed{V_0 = -2.5V}$$

$$= \Rightarrow V_0 = \left(1 + \frac{2}{1}\right) \times 2 = 3 \times 2 = 6V$$

$$\Rightarrow \boxed{V_0 = 6V}$$

$$3) V_0 = \frac{2 \times 3K}{3K + 3K} = 1V$$

$$V_0 = \frac{1 - 0}{6K} + \frac{1 - V_0}{6K} + 0 = D$$

$$\Rightarrow \boxed{V_0 = 2V}$$

$$4) \text{ Hence; } \frac{D - 5}{5K} + \frac{D - V_0}{4K} + 0 = D$$

$$\Rightarrow -\frac{35 - 5V_0}{5K} = 0 \Rightarrow -35 - 5V_0 = 0 \Rightarrow 5V_0 = -35$$

$$\Rightarrow \boxed{V_0 = -7V}$$

$$Q) \frac{0 - V_{in}}{3k} + \frac{0 - V_o}{5k} + 0 = 0$$

$$\Rightarrow V_o = -\frac{5}{3} V_{in}$$


$$= -\frac{10}{3} \sin 3t \text{ V}$$

Applying KVL:


$$-I_b + \frac{V_o - 0}{5k} + \frac{V_o - 0}{2k} = 0$$

$$\Rightarrow \frac{V_o}{5k} + \frac{V_o}{2k} = I_b$$
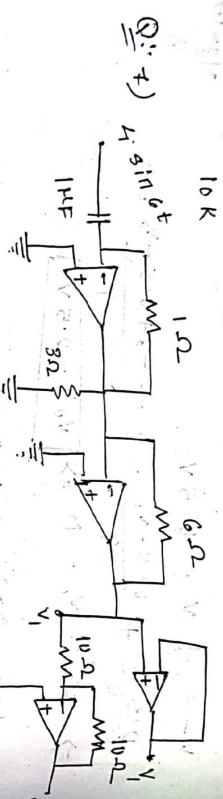
$$\Rightarrow I_b = \frac{4V_o}{10k} = \frac{-2}{3} \sin 3t \text{ mA}$$



Find relationship bet' V_1 & V_2 .

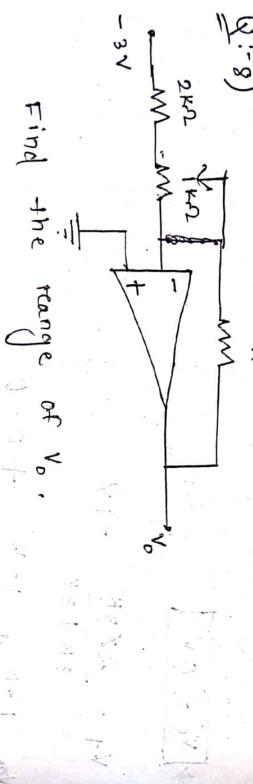

Find the range of V_o .

Ans:-


$$x) \frac{0 - V_2}{10} + \frac{0 - V_1}{10} = 0$$

$$\Rightarrow \frac{-V_2}{10} = \frac{V_1}{10}$$


or $\boxed{V_2 = -V_1}$

$$\begin{aligned} \frac{d}{dt} V_0 &= \frac{-1}{2} x^2 - 2 \\ V_r &= \frac{1}{2} x - 6 = \frac{x-12}{2} \end{aligned}$$

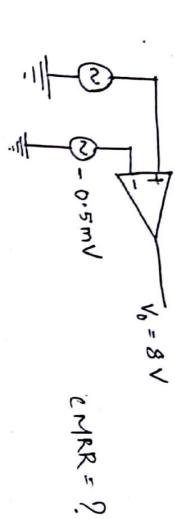Q: For an experimental set up, which op-amp is shown below:-



$$CMRR = ?$$

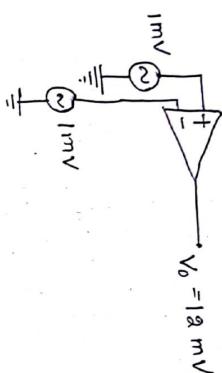

$$V_o = 12 \text{ mV}$$

$$CMRR = \frac{A_d}{A_c}$$

$$A_d = \frac{V_{id}}{V_{cd}} = \frac{8V}{V_1 - V_2} = \frac{8V}{8.5 + 0.5mV} = 8000$$

$$A_c = \frac{V_{oc}}{\left(\frac{V_1 + V_2}{2}\right)} = \frac{12 \text{ mV}}{1 \text{ mV}} = 12$$

CMRR = $\frac{8000}{12} \rightarrow$ Absolute state

$$CMRR|_{dB} = 20 \log_{10} \left(\frac{8000}{12} \right) \text{ dB}$$

Q: Determine the o/p voltage of Op-Amp for the

o/p voltage $V_o = 200 \mu\text{V}$, $V_a = 140 \mu\text{V}$. The amplifier has the differential gain $A_d = 6000$ and CMRR is 200.

$$V_{11} = 200 \mu\text{V}$$

$$V_{12} = 140 \mu\text{V}$$

$$CMRR = 200$$

$$Ad = 6000$$

$$V_{id} = V_{11} - V_{12} = 200 - 140 = 60 \mu A$$

$$\sqrt{ic} = \frac{V_{11} + V_{12}}{2} = 140 \mu V.$$

$$CMRR = \frac{Ad}{Ac} \\ \Rightarrow 200 = \frac{6000}{Ac} \\ \Rightarrow Ac = 30$$

$$Ad = \frac{V_{od}}{V_{id}} = \frac{V_{od}}{60 \mu V}$$

$$\Rightarrow V_{od} = 6000 \times 60 \mu V$$

$$= 360 mV.$$

$$Ac = \frac{V_{oc}}{V_{ic}} = \frac{V_{oc}}{140 \mu V}$$

$$\Rightarrow V_{oc} = 30 \times 140 \mu V = 5100 = 5.1 mV$$


$$V_D = V_{od} + V_{oc} \\ = 360 + 5.1 = 365.1 mV.$$

Slew Rate :-

This is the characteristics of op-amp and defined as max. rate of change of output with respect to input.

Mathematically, $SR \triangleq \left. \frac{dV_o}{dt} \right|_{\text{max.}} \left(\frac{\text{Volts}}{\mu s} \right)$

Q: Determine the slew rate;

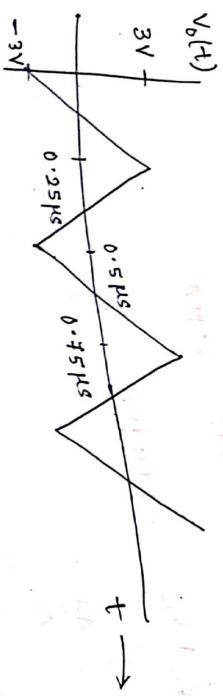

$$SR \triangleq \frac{6}{0.25} = 24 \text{ volt/μs}$$

Q: The slew rate of operational amplifier is

24 volt/μs

For the output of op-amp

$$V_o(t) = 5 \sin 2\pi f_0 t + V_0$$

Determine the frequency of o/p signal of

Op-Amp.

$$SR \triangleq = 24 \text{ volt/μs}$$



$$SR = \frac{dV_o}{dt} \Big|_{\text{max}}$$

$$= 10\pi f_0 \cos 2\pi f_0 t \Big|_{\text{max}}$$


$$24 \text{ volt/μs} = 10\pi f_0$$

$$f_0 = \frac{24}{10\pi} \times 10^6 \text{ Hz} = \frac{24}{\pi} \text{ MHz}$$

Significance of slew rate:

→ It is used to calculate the frequency of o/p signal and also used to calculate the maxm swing in o/p signal.

Write the block diagram of Op-Amp :-

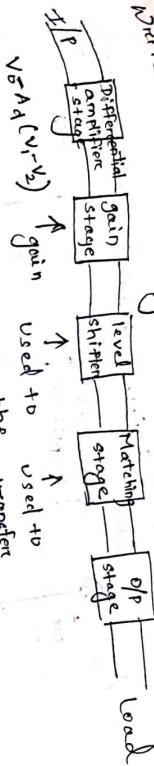

$v_{out}(v_1 - v_2)$ gain used to remove the dc part at the o/p of gain stage.

used to transfer power of level shifter to the o/p of op stage.

remove the dc part at the o/p of gain stage.

used to remove the dc part at the o/p of op stage.

remove the dc part at the o/p of op stage.

remove the dc part at the o/p of op stage.

remove the dc part at the o/p of op stage.

remove the dc part at the o/p of op stage.

remove the dc part at the o/p of op stage.

remove the dc part at the o/p of op stage.

remove the dc part at the o/p of op stage.

remove the dc part at the o/p of op stage.

remove the dc part at the o/p of op stage.

remove the dc part at the o/p of op stage.

remove the dc part at the o/p of op stage.

remove the dc part at the o/p of op stage.

remove the dc part at the o/p of op stage.

remove the dc part at the o/p of op stage.


remove the dc part at the o/p of op stage.

remove the dc part at the o/p of op stage.

Feedback Amplifier :-

25/11/19

(Block diagram of feedback network)

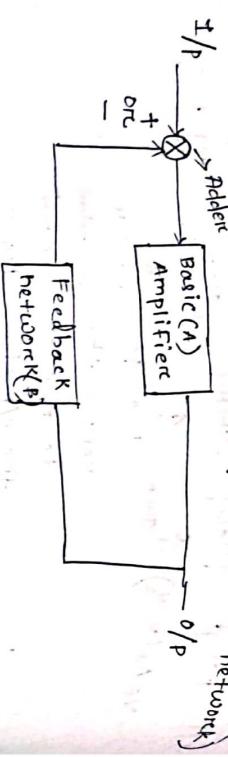


→ Feedback network is used to feedback circuit control the o/p of the system by adding or subtracting some part of o/p in the o/p

→ Types of feedback :-

(1) Negative Feedback :-

→ + is also known as degenerative circuit.

e.g:- All amplifiers

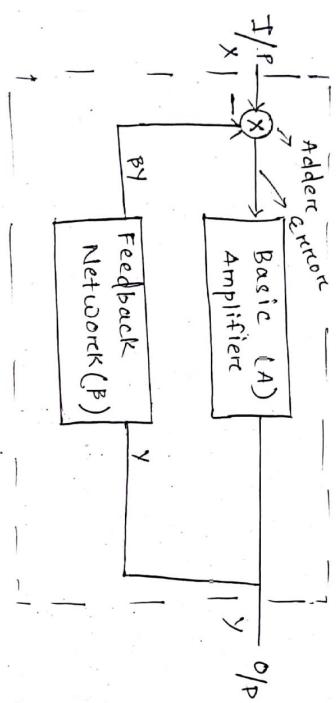

$$\text{error} = x - \beta y$$

$$y = A \cdot \text{error}$$

$$y = A(x - \beta y)$$

$$y = Ax - A\beta y$$

$$y + A\beta y = Ax$$

$$y(1 + A\beta) = Ax$$

$$\frac{y}{x} = \frac{A}{1 + A\beta}$$

= Gain of feedback
voltage amplifier

concept of -ve feedback:-

- All the o/p should be reached at the i/p of feed back (B) network, if the o/p is voltage the connection of B between i/p & B network and o/p connection must be in shunt / parallel.
- If the o/p is current, then the connection between i/p of B network and o/p must be in series .
- Input & output of B network are connected in such a manner that both will have significance .
- If the i/p is current, i/p & o/p of an B network must be connected in parallel .
- If the i/p is voltage i/p & o/p of B network must be in series .

-Ve feedback connection types. (Types of -Ve feedback amplifiers) :- (Topology)

→ There are 4 types of feedback amplifier

(i) Voltage amplifier


(ii) Current amplifier

(iii) Trans impedance

(iv) Trans conductance.

Voltage Amplifier :-

OR voltage-series or series-shunt.

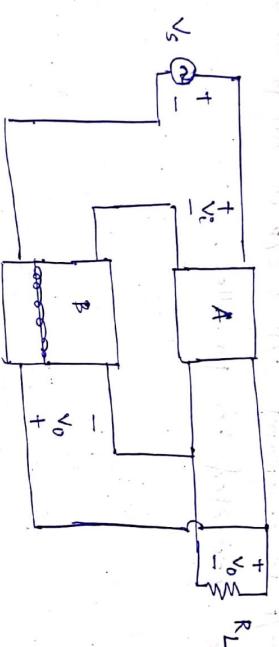

$$V_f = \beta V_o$$

Gain with feedback = $A_F \triangleq \frac{V_o}{V_s}$

$$A_F = \frac{V_o}{V_s}$$

Applying KVL at $\frac{1}{\beta}$,

$$V_s - V_i - V_f = 0$$

$$\Rightarrow V_s = V_i + V_f$$

$$\boxed{A_F = \frac{V_o}{V_s}}$$

$$A_f = \frac{V_o}{V_s}$$

$$= \frac{V_o}{V_i + V_f} =$$

$$= \frac{V_i}{V_i + V_f}$$

$$A_f = \frac{A}{1 + AB}$$

$$= \frac{A}{1 + \frac{V_f}{V_i}} = \frac{A}{1 + \frac{V_f}{V_i} \times \frac{V_o}{V_i}}$$

$$= \frac{V_i}{V_i + V_f}$$


Current Amplifier:
OR shunt-series OR current shunt

$$\frac{I/P}{I}$$

$$\frac{O/P}{I}$$

shunt

series

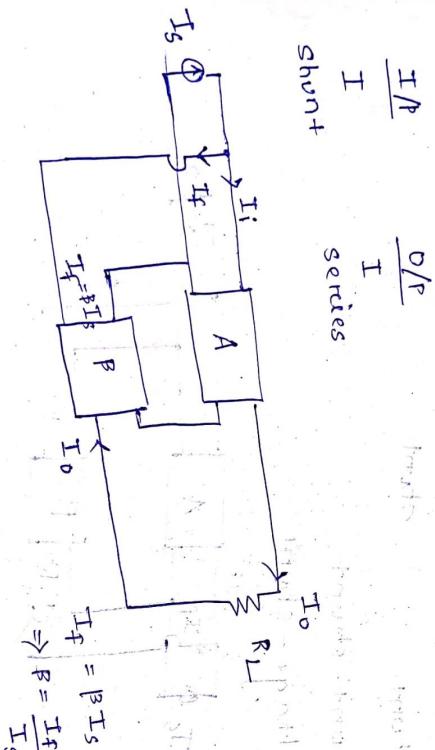

$$I_f = \beta I_s$$

$$I_f = \frac{I_o}{I_s}$$

$$A_f = \frac{I_o}{I_s}$$

Applying KCL at input

$$I_s = I_i + I_f$$

$$A_f = \frac{I_o}{I_i + I_f}$$

$$A = \frac{I_o}{I_i}$$

$$A_f = \frac{I_o}{I_i}$$

$$= \frac{A}{1 + A\beta}$$

$$= \frac{A}{1 + \frac{I_f}{I_o} \times \frac{I_o}{I_i}} = \frac{A}{1 + \beta A + 1} = \frac{A}{\beta A + 2}$$

$$A_f = \frac{A}{1 + A\beta}$$

Trans - impedance :-

$$\frac{I_o}{I_i}$$

V

shunt

Name :- shunt-shunt

Voltage - shunt



$$I_f = \beta V_o \Rightarrow \beta = \frac{I_f}{V_o}$$

$$\text{Hence, } A_f = \frac{V_o}{I_i}$$

Applying KCL at I/P

$$I_s = I_i + I_f$$

$$A_f = \frac{V_o}{I_i + I_f}$$

$$= \frac{V_o}{I_e}$$

$$= \frac{I_i + I_f}{I_e}$$

$$= \frac{A}{I_i}$$

$$= \frac{A}{I_i + I_f} \cdot \frac{V_o}{I_i}$$


$$A_f = \frac{A}{1 + A\beta}$$

Trans-conductance :-

(series-series or current series)

$$\frac{I/P}{V} = \frac{O/P}{I}$$

series

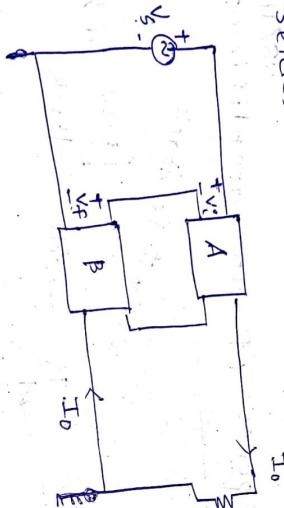

$$A_f = \frac{I_o}{V_s}$$

Applying KVL at I/P;

$$V_s = V_i + V_f$$

$$A_f = \frac{I_o}{V_i} = \frac{I_o}{V_i + V_f}$$

$$A_f = \frac{V_s}{V_i} = \frac{V_i + V_f}{V_i}$$

$$\Rightarrow A_f = \frac{A}{1 + A\beta}$$

$$= \frac{A}{1 + \beta A} \cdot \frac{I_o}{V_i}$$

$$= \frac{A}{1 + \beta A}$$

$$A_f = \frac{A}{1 + \beta A}$$

$\boxed{\text{I/P imp.}}$


* Voltage Amplifier $\rightarrow A_{v_f} = \frac{A_v}{1 + A\beta} \uparrow Z_{i_f} = Z_i(1 + \beta)$

* Current Amplifier $\rightarrow A_{i_f} = \frac{A_i}{1 + A_i\beta} \downarrow Z_{i_f} = \frac{Z_i}{1 + A\beta}$

* Transistor Amplification $\rightarrow A_{z_f} = \frac{A_z}{1 + A_z\beta} \downarrow Z_{i_f} = \frac{Z_i}{1 + A\beta}$

* Transconductance $\rightarrow A_{g_f} = \frac{A_g}{1 + A\beta} \uparrow Z_{i_f} = Z_i(1 + \beta)$

Frequency response of an amplifier:

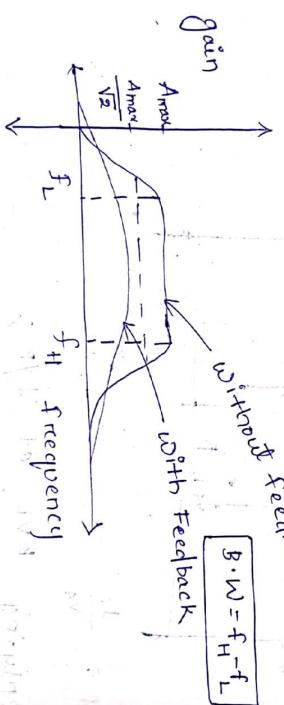

* Note :-
Gain $\downarrow \times B \cdot \omega \uparrow = \text{constant}$

$B \cdot \omega_f = (1 + A\beta) B \cdot \omega$
The B·ω of amplifier will increase the

amplifier with -ve feedback by factor of $(1 + A\beta)$

term.

Distortion (Noise):-

$$D_f = \frac{D}{1 + A\beta}$$

Advantages:- Negative feedback produces the stable output by reducing the gain.

O/P imp.

$$A_f = \frac{A}{1 + A\beta}$$

$$\downarrow Z_{of} = \frac{Z_o}{1 + A\beta}$$

$$\uparrow Z_{of} = \frac{Z_o(1 + A)}{1 + A\beta}$$

$$\downarrow Z_{of} = \frac{Z_o}{1 + A\beta}$$

$$\uparrow Z_{of} = Z_o(1 + A\beta)$$

$A_f \rightarrow$ Gain with feedback
 $A \rightarrow$ Gain without feedback
 $\beta \rightarrow$ Feedback factor

$A\beta \rightarrow$ Closed loop gain.

\rightarrow Negative feedback enhances
 the O/P impedance of voltage

\rightarrow -ve feedback reduces the O/P impedance of

amplifier.
 $Z_{if} = Z_i(1 + A\beta)$
 voltage amplifier.

$$Z_{of} = \frac{Z_o}{1 + A\beta}$$

$$Z_{if} = (1 + A\beta) Z_i$$

\rightarrow -ve feedback enhances the $B \cdot \omega|_f = (1 + A\beta) B \cdot \omega$

\rightarrow -ve feedback reduces the noise (distortion).

\rightarrow -ve feedback reduces

$$D_f = \frac{D}{1 + A\beta}$$

\rightarrow -ve voltage feedback is applied to an

Q When -ve voltage feedback is applied overall

amplifier with gain (A) = 1000. Overall

gain false to $A_f = 6$. calculate the feedback

gain factor (β) ?

factor?

Ans :-

$$A = 1000$$

$$A_F = 6$$

Hence, $A_F = \frac{A}{1 + A\beta}$

$$\Rightarrow 6 = \frac{1000}{1 + 1000\beta}$$

$$\Rightarrow 6 + 6000\beta = 1000$$

$$\Rightarrow 6000\beta = 1000 - 6$$

$$\Rightarrow \beta = \frac{1000 - 6}{6000} = \frac{994}{6000} = 0.16$$

Q: If the gain & distortion of an amplifier are 150 & 5% respectively without feedback & the stage has 10% of its o/p voltage apply as -ve feedback, Find the distortion of amplifier with -ve feedback.

Ans :- $A = 150$

$$D = 5\%$$

$$\beta = 10\% = \frac{1}{10}$$

$$D_F = \frac{D}{1 + A\beta} = \frac{5\%}{1 + 150 \times \frac{1}{10}} = \frac{5\%}{16} = 0.003.$$

Q: Determine the voltage gain, i/p & o/p impedance with feedback for a voltage series feedback having $A = -100$, $R_i = 10k\Omega$, $R_o = 20k\Omega$.

(a) $\beta = -0.1$

(b) $\beta = -0.5$

(a) $A_F = \frac{A}{1 + A\beta} = \frac{-100}{1 + (-100)(-0.1)} = \frac{-100}{101} = -0.99$

$$\pi_{if} = \pi_i(1 + A\beta) =$$

$$\pi_{of} = \frac{\pi_o}{1 + A\beta} =$$

Q: If an amplifier with gain $A = -1000$, with $\beta = -0.1$ has a gain change of 20%. due to temperature. Calculate the change in gain of calculate feedback.

Ans:

$$A = -1000$$

$$\beta = -0.1$$

$$A_f = \frac{A}{1 + A\beta}$$

$$\frac{dA_f}{dA} = \frac{(1 + A\beta)1 - A(\beta)}{(1 + A\beta)^2} = \frac{1}{(1 + A\beta)^2}$$


$$dA_f = \frac{dA}{(1 + A\beta)^2} = \frac{20\%}{1 + (-1000)(-0.1)} = \frac{20\%}{1 + 100}$$

$$= \frac{\frac{1}{100}}{\frac{105}{100}} = \frac{1}{505} = 0.0019$$

Wednesday.

02/12/19

①

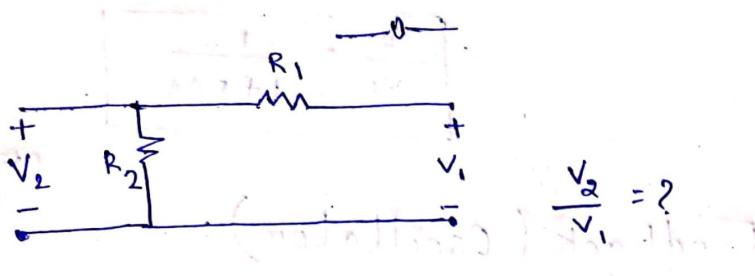

$$\frac{\frac{1}{R_1+R_2}}{\frac{1}{R_1+R_2}}, \frac{R_2}{R_1+R_2}$$

In series, voltage division occurs.

$$V_2 = \frac{V_1 R_2}{R_1 + R_2}$$

$$\Rightarrow \frac{V_2}{V_1} = \frac{R_2}{R_1 + R_2}$$

* Impedance offered by

capacitor, $\frac{1}{j\omega C} = \frac{1}{2\pi f C}$

inductor, $= j\omega L = \text{ohm}$

resistor, $= R$.

$L = 1 \text{ Henry}$.


$V_{in} = 0 \text{ ohm}$

$$i, j = \sqrt{-1}$$

$$* Z_C = \frac{1}{j\omega C} = \frac{-1}{\omega C} = \frac{1}{CS} (\Omega)$$


$$* Z_L = j\omega L = LS (\Omega)$$

$$* Z = R + jX$$

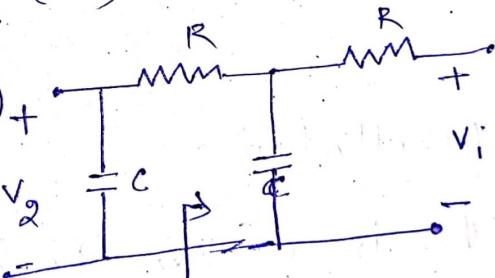

$$* S = \sigma + j\omega$$

NOTE :-

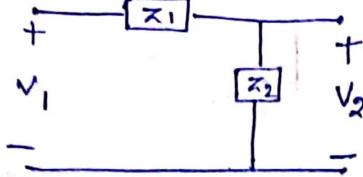

$$\frac{V_2}{V_1} = \frac{Z_2}{Z_1 + Z_2}$$


$Z = \text{Impedance}$

$$\Rightarrow V_2 = \frac{V_1 \times \frac{1}{CS}}{R + \frac{1}{CS}} = \frac{V_1}{RCS + 1}$$

$$\frac{V_2}{V_1} = \frac{1}{1 + RCS}$$

05/12/2019

Positive Feedback (Oscillator) :-

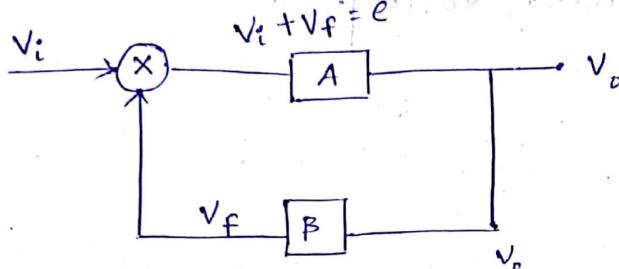

$$\beta = \frac{V_f}{V_d}$$

$$e \rightarrow \text{error} \cdot \frac{V_d}{e} = A$$

$$V_f = \beta V_d \Rightarrow V_d = eA = (V_i + V_f)A$$

$$= V_i A + \beta V_d A$$

$$V_d (1 - A\beta) = V_i A$$

$$A_f = \frac{V_d}{V_i} = \frac{A}{1 - A\beta}$$

Oscillator :-

It is a +ve feedback circuit in which there is no external input is applied and its generate and produces a sino-sodial signal (single frequency component).

Sustain Oscillators :-

When the O/P signal is a sinusoidal with one frequency and the peak amplitudes are fixed that signal is known as sustain oscillated signal.

Condition for sustain oscillation :-

(Bark Hansen's criterion of principle)

$$Af = \frac{A}{1 - AB}$$

$$1 - AB = 0$$

$$AB = 1 = 1 + j0 = 1 \underbrace{[0^\circ \text{ or } 360^\circ]}$$

$$|AB| = 1, \angle AB = 360^\circ$$

$$i = j = \sqrt{-1}$$

$$|z| = \sqrt{x^2 + y^2}, \theta = \tan^{-1} \left| \frac{y}{x} \right|$$

$$z = x + iy$$

$$= |z| e^{j\theta}$$

$$= |z| \angle \theta$$

$\beta \rightarrow$ May be real or may be complex.

$$\tau = 1 + j1$$

$$= \sqrt{2} \angle 45^\circ$$

$$\tau = j = 0 + j1$$

$$= 1 \angle 90^\circ$$

$$\tau = 1 + j0$$

$$= 1 \underbrace{[0^\circ \text{ or } 360^\circ]}$$

$\beta \rightarrow$ Feedback factor / Gain of β network.

$A \rightarrow$ Gain of basic amplifier / Gain without feedback

$AB \rightarrow$ Loop gain.

Principles :-

1. Magnitude of loop gain = 1 (loop gain) (magnitude condⁿ)
 $|AB| = 1$

2. Phase of loop gain = 360° . (loop gain) (phase condⁿ)
 $\angle AB = 360^\circ$

3. $B = \beta_{rc} + j\beta_i$ (loop gain) (standard form)
 For sustain oscillator,

$$A\beta = 1$$


$$A(\beta_{rc} + j\beta_i) = 1$$

$$\text{Im}(B) = \beta_i = 0 \quad (\text{It must be } 0)$$


Procedure to calculate frequency of oscillation (ω_0, f_0)

→ calculate β .

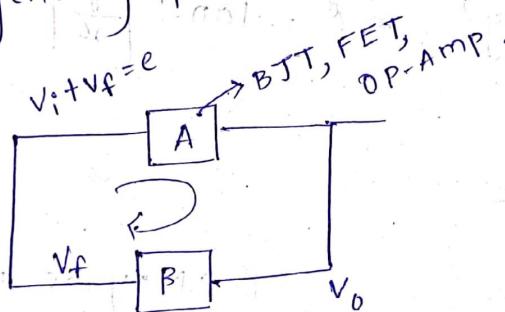→ Put imaginary part of B to calculate B, f_0 .



RC phase shift oscillator:-

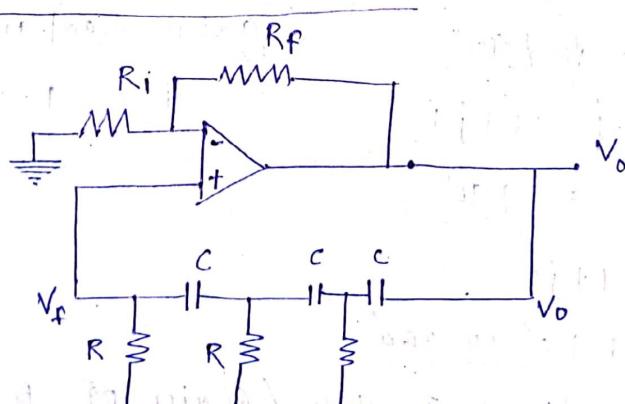


Amplification condition
 Condition about feedback per stage to maintain
 condition

Note :-

$$Z_C = \frac{1}{j\omega C} = \frac{1}{sC}$$

$$Z_L = j\omega L = sL$$

$$Z_R = R$$

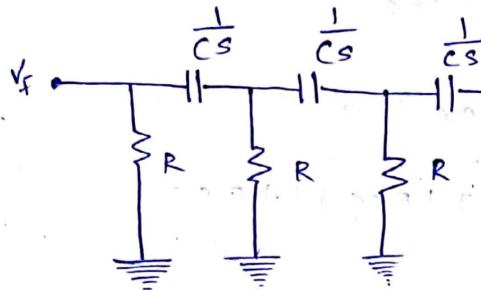


Q.1	1 mark.
2	
3	
4	
5	
6	
7	
8	
9	
10	

2 mark


Lq.

Derivation of frequency of oscillator:-
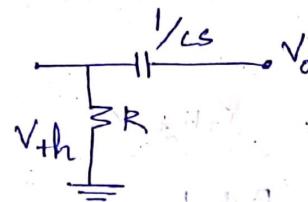
$$\begin{aligned} V_{th1} &= \frac{V_o \times R}{R + \frac{1}{CS}} \\ &= \frac{V_o RCS}{RCS + 1} \end{aligned}$$




$$\underline{R_{th1}}$$

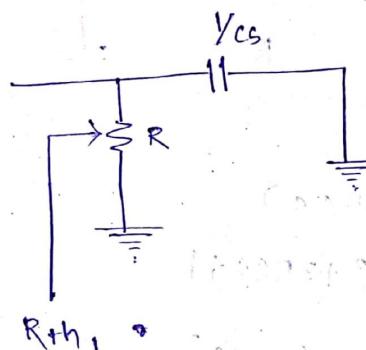

$$\underline{R_{th1}} = \frac{R \times \frac{1}{CS}}{R + \frac{1}{CS}}$$
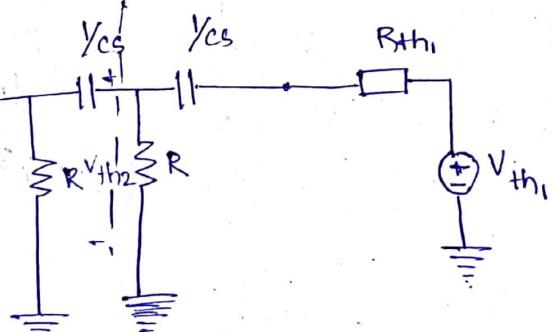
$$\begin{aligned} V_{th2} &= \frac{V_{th1} R}{\frac{1}{CS} + \frac{R}{R_{th1}} + R} \\ &= \frac{V_o RCS \cdot R}{1 + RCS} \end{aligned}$$




$$\frac{1 + RES + RCS + (RCS)^2 + RCS}{CS(1 + RES)}$$

$$= \frac{V_o (RCS)^2}{(RCS)^2 + 3RCS + 1}$$

$$R_{th2} = R \left(\frac{1}{CS} + \frac{R}{RCS+1} \right)$$

$$= R + \frac{1}{CS} + \frac{R}{RCS+1}$$
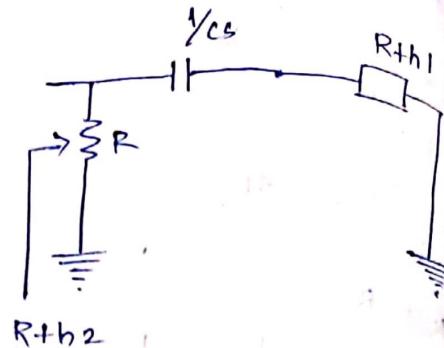
$$R_{th2} = \frac{R(RCS+1+RCS)}{(RCS)^2 + RCS + RCS + 1 + RCS}$$




$$= \frac{R(1+2RCS)}{(RCS)^2 + 3RCS + 1}$$

$$V_f = \frac{V_{th2} \times R}{R + \frac{1}{CS} + R_{th2}}$$

$$= \frac{V_o (RCS)^2}{(RCS)^2 + 3RCS + 1}$$
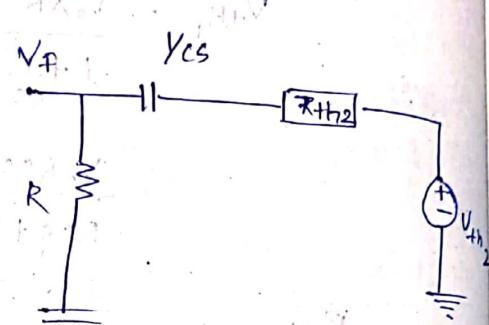
$$= \frac{R + \frac{1}{CS} + R(1+2RCS)}{(RCS)^2 + 3RCS + 1}$$



$$\begin{aligned} s &= j\omega \\ s^2 &= -\omega^2 \\ s^3 &= -j\omega^3 \end{aligned}$$

$$\beta = \frac{V_f}{V_o} = \frac{(RCS)^3}{(RCS)^3 + 3(RCS)^2 + RCS + (RCS)^2 + 3RCS + 1}$$

$$= \frac{(RCS)^2}{(RCS)^3 + 6(RCS)^2 + 5RCS + 1}$$

$$= \frac{1}{1 + \frac{6}{RCS} + \frac{5}{(RCS)^2} + \frac{1}{(RCS)^3}}$$

$$= \frac{1}{1 - \frac{jG}{RCS} - \frac{5}{R^2 C^2 \omega^2} + j \frac{1}{R^3 C^3 \omega^3}}$$

$$\Rightarrow \beta = \frac{1}{1 - \frac{5}{R^2 C^2 \omega^2} - j \left(\frac{G}{RC\omega} - \frac{1}{R^3 C^3 \omega^3} \right)}$$

For sustain oscillation,

$$\frac{G}{RC\omega} - \frac{1}{R^3 C^3 \omega^3} = 0$$

$$\Rightarrow \frac{G}{RC\omega} = \frac{1}{R^3 C^3 \omega^3}$$

$$\Rightarrow G R^2 C^2 \omega^2 = 1$$

$$\Rightarrow \omega^2 = \frac{1}{G R^2 C^2}$$

$$\Rightarrow \omega = \frac{1}{\sqrt{G} RC}$$

$$\Rightarrow F_0 = \frac{1}{2\pi\sqrt{G} RC}$$

$$AB_{rc} = 1$$

$$\Rightarrow A \frac{1}{1 - \frac{5}{R^2 C^2 \omega^2}} = 1$$

$$\Rightarrow A = 1 - \frac{5}{R^2 C^2 \omega^2}$$

$$\Rightarrow A = 1 - \frac{5}{R^2 C^2 \times \frac{1}{G R^2 C^2}} = 1 - 3.0 = -2.0$$

$$\Rightarrow A = -2.0$$

(60)